



TRANSIENT SURGE FILTERING

USE OF LOW PASS FILTERING IN SURGE PROTECTION





AGENDA

- Classification of Impulses & Surges
- Traditional MOV/Crowbar Protection vs. Filtering
- Concepts Behind Surge Filtering
- Summary





Classifications of Surge Impulses

- Waveshape
 - t_{front}, t_{tail}
- Magnitude

$$-i_{pk}$$

Charge
Q

$$|^{2}t$$

- kJ/Ω







Classification of Surge Impulses (cont.)

- Frequency
 - Harmonics

- $\hat{f}(\xi) = \delta(0) + \delta(10E3) + \delta(20E3) + ... + \delta(100E3)$
- Sum of Dirac delta functions
- Bandwidth
- Magnitude



All transients are signals and can be analyzed by the Fourier Transform





Traditional Surge Protection Design

• Metal Oxide Varistors (voltage limiting devices)



Voltage limiting and switching are the main components for protection





Traditional Surge Protection Design

- Cascading protection
 - SPDs at the service entrance are higher rated (higher let-through)
 - SPDs at the sub-panels are lower rated (lower let-through)



Cascading protection limits the voltage from transients in stages





Cascading Stage Limiting



Each stage diverts more energy and keeps the end voltage low





Different Voltages on Parallel Lines



Voltages in parallel are the same, additional voltage drop exists





Voltage Must be Dropped Across the Wiring



Wiring impedance can be used to isolate staged protection





Voltage Drop Across Wiring

- Theoretically: 4mm² (12AWG) wire is $\approx \frac{4m\Omega}{m}$ and $\frac{1\mu H}{m}$
- $V = i \cdot R + L \frac{di}{dt}$ K^{1} M^{1} M^{2} K^{1} M^{2} K^{1} M^{2} K^{1} M^{2} K^{1} M^{2} K^{1} $K^$
- Gets lower with larger wire

		6 AWG		4 AWG		2 AWG	
		(V/ft)	(V/cm)	(V/ft)	(V/cm)	(V/ft)	(V/cm)
3	kΑ	152.40	5.00	94.45	3.10	83.61	2.74
10	kΑ	441.16	14.47	385.00	12.63	340.65	11.18
40	kΑ	?	?	1579.35	51.82	1254.19	41.15

Wiring might be sufficient to mitigate this problem





When Wiring is Short with Minimum Losses (1/2)

Smaller SPD clamps first

Since the lower rated MOVs are more sensitive they will begin clamping the voltage first

Larger SPD only when threshold is exceeded

The larger SPD will only turn on if the smaller SPDs clamping voltage goes above the turn-on voltage of the larger SPD





Current initially goes through the smaller SPD until larger turns on





When Wiring is Short with Minimum Losses (2/2)



The lower rated device absorbs most of the impulse





What is a Low Pass Filter?

Low-Pass Filter

• Lower frequencies Pass while higher frequencies are attenuated



Low Frequency Signals Pass!





Low Pass Filters

Low frequency signals experience no attenuation • Corner Frequency Gain = 20 log $\frac{Vout}{Vin}$ fc High frequency signals experience Stop Band Pass Band ٠ 0dB large amounts of attenuation -3dB (45°) -3dB Frequency Slope = Response -20dB/Decade Output I R Bandwidth V_{in} V_{c} *f*c (LP) Frequency (Hz) Phase (Logarithmic Scale) 00 $H(s) = \frac{1}{1 + RCs}$ -45° Phase Shift Where s = $j\omega$ -90° Frequency (Hz)





Characterizing a Filter

- At higher frequencies, Vout is multiplied by something smaller than "1".
- 3 dB Point "cutoff frequency" this is the frequency where the filter cuts off of the output power (half-power point)
- 100 kHz Gain a benchmark frequency used to compare filtering at a high frequency



Higher Frequencies are attenuated!



100kHz Benchmark



- = 20 * Log(0.0086/15.8)
- = 20 * Log(0.0005)
- = -65.28 dB





- Filter input = 15.8Vpp
- Filter output = 8.6mVpp



Industry rule of thumb is for -45db at 100kHz





10⁵

RC Filter







LC Filter









Comparing: RC vs LC







Combining these Functions



Low-Pass between LINE and NEUTRAL

Traditional Surge Protective Device (MOV, GDT...)





Combining these Functions

- Clamps transient voltage
- Slows the rate of voltage rise
- Attenuates small signal RFI/EMI noise problems



Surge Filter reduces let-through voltage!





Value Choices for inductor & capacitor Filter – Negligible improvement but badly ringing

- 3kA 8/20us
- Green SPD output
 - 378Vpk
- Purple filter output
 - 620Vpk





- No improvement over MOV only
- Harmful ringing of the LC filter actual makes the results worse

Filter ringing worsens results!





Value Choices for inductor & capacitor

Filter – Bad

- 3kA 8/20us
- Green SPD output
 - 370Vpk
- Purple filter output
 - 542Vpk



- Filter starts to improve the dV/dt
- The output voltage is still climbing even after MOV voltage has dropped.
- Once the inductor current reaches zero the output voltage peaks

Voltage continues to rise after MOV drops



Value Choices for inductor & capacitor

Filter – Good not Great

Protection Engineers Group

- 3kA 8/20us
- Green SPD output
 - 378Vpk
- Purple filter output
 - 358Vpk



- Filter starts to improve the dV/dt
- The output voltage is still climbing even after MOV voltage has dropped.
- Once the inductor current reaches zero the output voltage peaks

What is the point?





Value Choices for inductor & capacitor

Filter – Great Filter

- 3kA 8/20µs
- Green SPD output
 - 382Vpk
- Purple filter output
 - 166Vpk





- Filter significantly reduced the dV/dt
- Filter output is less than the MOV alone

Filter reduces the output!





Cascading Stage Testing w/ TSF







Cascading Stage Testing w/ TSF







Cascading Stage Testing w/ TSF



Each stage diverts more energy and keeps the end voltage low





Many industries demand high performance protection

- •Process Control
- •SCADA and Telemetry
- •Panel Shops / Sl's
- •OEMs
- •Automotive
- •Petrochem
- •Telecom Power
- •Lighting Control
- •Water & Wastewater Treatment
- •Medical Equipment
- •Semiconductor Equipment







Many Applications...





Application: BTS Sites

Mobile Telecom Enclosure

- Standalone type BTS sites
- No shelters trending upward
 - Small IP66 enclosure where they can fit all electrical switchgear equipment.



Example Application: Telecom BTS Sites





Application: Communication System at a LNG Extraction Facility

Telecommunications cabinets (Fiber nodes, telephones, CCTV)



Surge Filter (240VAC - 6A)





Example Application: Resource Extraction Telecom Cabinets





Application: Public Transit Pass

Fast Pass Reader for railway / subway stations



Fast Pass Reader



Surge Filter (120VAC - 20A)

Example Application: Railway Pass Readers





Application: SCADA

Remote Terminal Unit (RTU) used to take sections of the grid offline



Example Application: RTU





Application: Lighting Control

Lighting Control Panel



Example Application: Control Panel





Technology is not limited to small current levels







What is a Surge Filter?

Relevant Standards for Surge Filters

- UL 1449 4th Edition Standard for Surge Protective Devices
- UL 1283 Standard for Electromagnetic Interference Filters
- IEC 61643-11 Standard for Low-voltage Surge Protective Devices



RELEVANT STANDARDS!





QUESTIONS?

GREG.MARTINJAK@PENTAIR.COM

CHRISTIAN.BARCEY@PENTAIR.COM